

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
```

```
entity william is
```

```
port (KENDATAV, RD, WR, TAMPER, PANIC, DAJAR: in std_logic; LCDCOM: inout std_logic_vector (1 downto 0); ADDIN: inout
LCDENAB, KEYINT, KEYOUTEN, RAMOE, ADCEN, RAMWEN, TALRM, PALRM, DALRM, ALARM, ADCSTRT: inout std_logic; CLK0: in std_log
--IPT--
```

```
attribute LOC: string;
attribute LOC of CLK0: signal is "P11";
attribute LOC of TAMPER: signal is "P43"; ----IPT from switch
attribute LOC of PANIC: signal is "P42"; ----IPT from switch
attribute LOC of DAJAR: signal is "P41"; ----IPT from switch
attribute LOC of ADDIN: signal is "P27 P28 P29 P30 P31 P36 P37 P38"; ----IPT from Address bus
attribute LOC of WR: signal is "P39"; --IPT from /WR from MCU
attribute LOC of RD: signal is "P40"; --IPT from /RD from MCU
attribute LOC of KENDATAV: signal is "P3"; --IPT from Keypad Encoder
--OPT--
```

```
attribute LOC of LCDCOM: signal is "P16 P15"; --OPT to LCD command pins RW and RS
attribute LOC of LCDENAB: signal is "P17"; --OPT to LCD Enable pin
attribute LOC of KEYINT: signal is "P2"; --OPT to MCU /INT0
attribute LOC of KEYOUTEN: signal is "P4"; --OPT to Keypad Encoder
attribute LOC of RAMOE: signal is "P5"; --OPT to RAM READ ENABLE
attribute LOC of RAMWEN: signal is "P6"; --OPT to RAM WRITE ENABLE
attribute LOC of ADCEN: signal is "P7"; --OPT to ADC out put enable
attribute LOC of TALRM: signal is "P19"; --OPT code bit to MCU
attribute LOC of DALRM: signal is "P20"; --OPT code bit to MCU
attribute LOC of PALRM: signal is "P21"; --OPT code bit to MCU
attribute LOC of ALARM: signal is "P18"; --OPT to Alarm Interrupt on MCU
attribute LOC of ADCSTRT: signal is "P24"; --OPT ADC Start pin from MCU
end;
```

```
architecture behavioral of william is
```

```
--SIGNAL--
signal tamperq: bit;
--signal tamperqnot: bit;
signal panicq: bit;
--signal panicqnot: bit;
signal dajarq: bit;
--signal dajarqnot: bit;
signal avaqnot: bit;
signal avaq: bit;
--signal swts: in std_logic_vector (0 to 3);
```

```
--The following are the VHDL D Flip Flops used to debounce
--the alarm activation switches

--This is the Tamper switch debounce. It uses the rising edge of
--CLK0 to determine if the q output can change or not.
--The qnot output is not used and is commented out in the signal section
begin
  process
  begin
    wait until rising edge(CLK0);--use tamperqnot
    if TAMPER='1' then
      tamperq<='1';
    else
      tamperq<='0';
    end if;

  end process;
  --Next is the panic switch debounce. It works in much the same way as the
  --tamper debounce. Again, qnot is not used and is disregarded.
  process
  begin
    wait until rising_edge(CLK0);--use panicq
    if PANIC='1' then
      panicq<='1';
    else
      panicq<='0';
    end if;

  end process;
  --The Door ajar switch is exactly like the other two switches.
  process
  begin
    wait until rising edge(CLK0);--use dajarqnot
    if DAJAR='1' then
      dajarq<='1';
    else
      dajarq<='0';
    end if;

  end process;
  -----
  --Alarm Decode to MCU
  -----
```

```

--This section decodes the alarm switches to give a code word to the 8051.
--It uses the q outputs of the D Flip-Flop to control an output pin to the
--8051. The 8051 will check its pins to determine the alarm that was pushed.
--This is done for every alarm switch.
process(panicq,dajarq,tamperq)
begin
if tamperq='0' then TALRM<='1';
else TALRM<='0';
end if;

if panicq='1' then PALRM<='1';
else PALRM<='0';
end if;

if dajarq='0' then DALRM<='1';
else DALRM<='0';
end if;

if TALRM='1' or PALRM='1' or DALRM='1' then ALARM<='0';
else ALARM<='1';
end if;
end process;
-----
--LCD Address Decode

--This is the most complicated of the Address decodes. The LCD needs different
--commands to perform its functions. This is accomplished decoding the input address
--from the 8051. The commands that the LCD performs is determined by the input address.
--There are three different commands in use for the LCD shown by the three different
--states that LCDCOM can obtain (01 = write, 10 = read, 00 = command).
process (ADDIN)
begin
if ADDIN= "00010000" then LCDCOM<= "01";
elsif ADDIN= "00010001" then LCDCOM<= "10";
elsif ADDIN= "00010010" then LCDCOM<= "00";
else LCDCOM<="11";
end if;
end process;

--This portion is where the LCD enable gets clocked. The enable must be clocked after
--every command sent to it. To send this pulse, the CPLD simply XOR's the 8051 WR and RD
--signals together after it determines that LCDCOM received a proper command. Thus a
--small pulse is generated.
process (LCDCOM,WR,RD)
begin
if LCDCOM="01" then LCDENAB<=(WR xor RD);
elsif LCDCOM="10" then LCDENAB<=(WR xor RD);
elsif LCDCOM="00" then LCDENAB<=(WR xor RD);
else LCDENAB<='0';

```

```
end if;
end process;

--Keypad Address Decode

--This is the decode responsible for enabling the keypad encoder
--to place its information on the data bus. Note that this will only happen
--when the 8051 uses a movx command that will read ie: movx A,@DPTR
process (ADDIN,RD)
begin
if ADDIN="01000000" and RD='0' then KEYOUTEN<='0';
else KEYOUTEN<='1';
end if;
end process;

--The next process is a D Flip-Flop that helps to slow down the Key flutter coming
--from the encoder if the key is slowly let up. The qnot output from this
--Flip-flop directly drives the 8051 INT0.
process
begin
    wait until rising edge(CLK0);
    if KENDATAV='1' then
        avaq<='1';
    else
        avaq<='0';
    end if;
    avaqnot <= not avaq;
end process;
process (avaqnot)
begin
if avaqnot='0' then KEYINT<='0';
else KEYINT<='1';
end if;
end process;

---ADC DECODE
--This process decodes the address from the 8051 to either start an ADC
--conversion, or to enable the output from the ADC0808CCN. The enable pulse
--is based on a simple Anding of the proper address and the RD signal from the
--8051. The start is a bit more complicated in that the pulse generated comes
--from the XOR of RD and WR (much like the LCD) due to the timing needed for
--the pulse.
process (ADDIN)
begin
if ADDIN="00110000" and RD='0' then ADCEN<='1';
else ADCEN<='0';
end if;
```

```
if ADDIN="001111000" then ADCSTRT<=(WR xor RD);
else ADCSTRT<='0';
end if;
end process;

---RAM DECODE
--This is a simple decode that enables the RAM chip based on the ANDing
--of the RD or the WR to the input address. If its RD thats ANDEd, then
--the 8051 is calling for a read from the RAM. If it is WR that is ANDEd,
--then the 8051 is trying to write to the RAM chip
process (ADDIN,RD)
begin
if ADDIN="00100000" and RD='0' then RAMOE<='0';
else RAMOE<='1';
end if;
end process;
process (ADDIN,WR)
begin
if ADDIN="00100000" and WR='0' then RAMWEN<='0';
else RAMWEN<='1';
end if;
end process;
end behavioral;
```